

CPSC 2610
Lab Assignment 3
Quoc Ho

1.


a. Truth Table

x	y	E
0	0	1
0	1	0
1	0	0
1	1	1


b. Boolean Expression:

$$E = x'y' + xy$$

c.

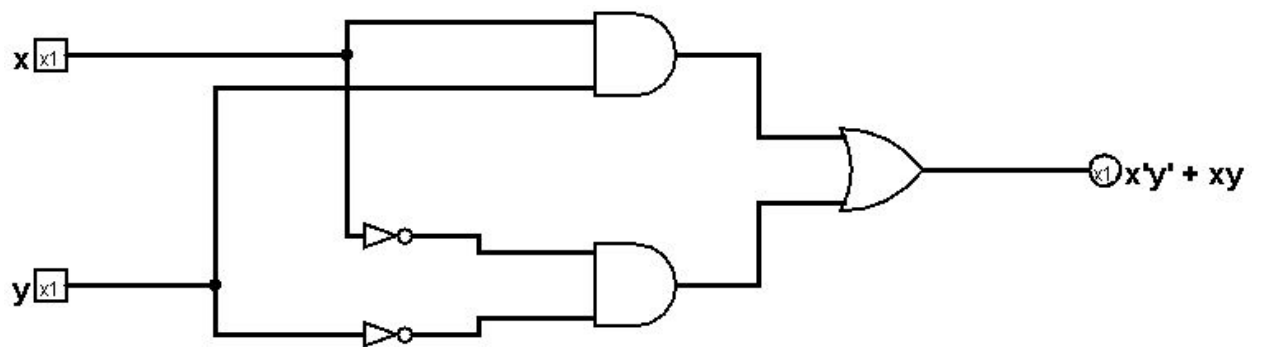

d.

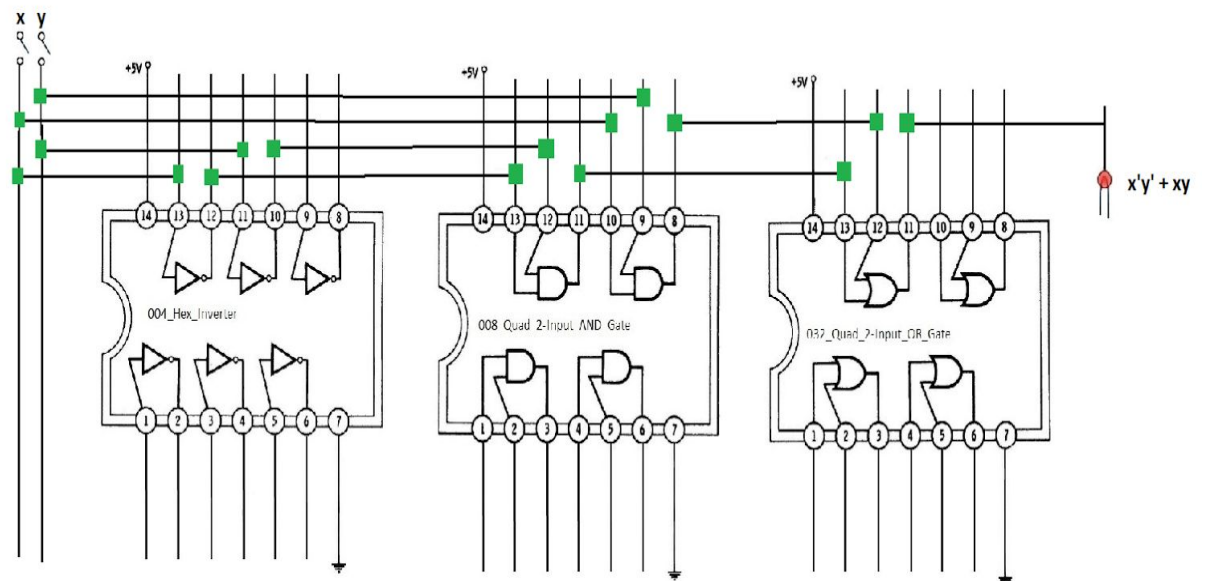

2.

a.

x	y	A	B	C	D
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

b. Boolean Expression


$$A = x'y'$$

$$B = x'y$$


$$C = xy'$$

$$D = xy$$

c.

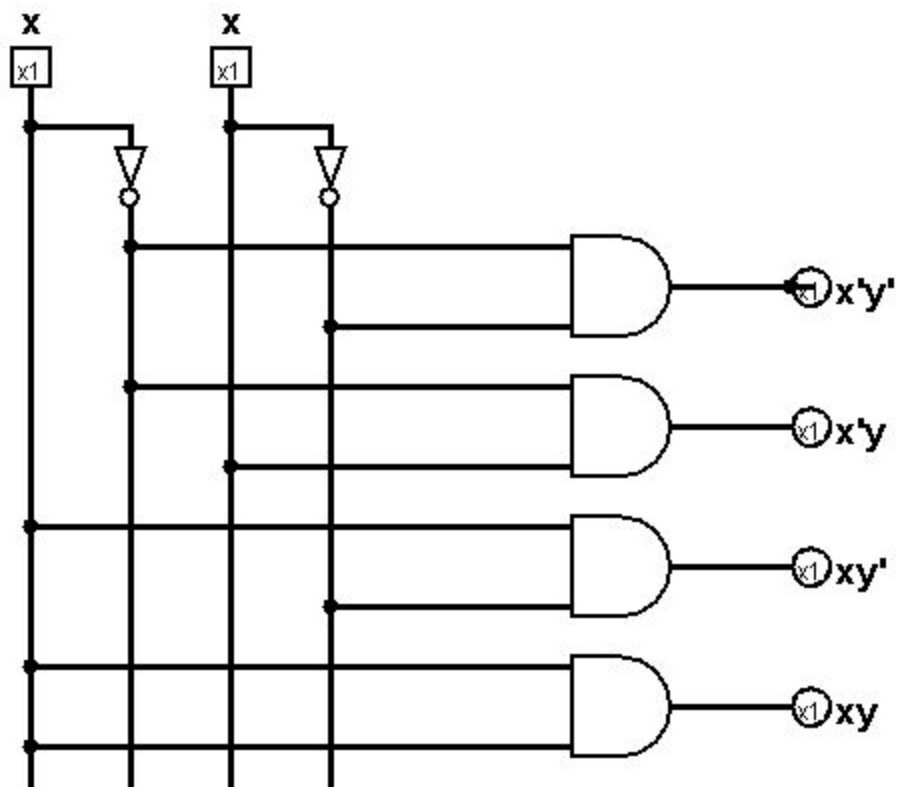

d.

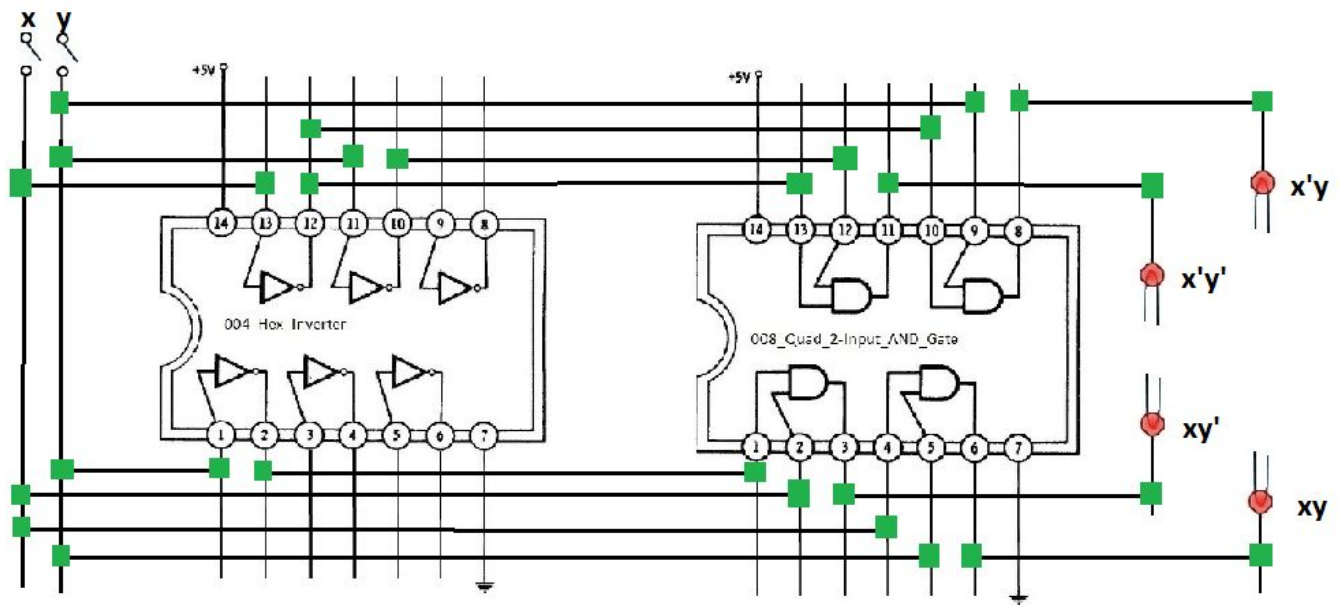

3.
a.

x	y	z	A1	A2	A3	A4	A5	A6	A7	A8
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

b. Boolean Expressions:

$$A1 = x'y'z'$$

$$A2 = x'y'z$$

$$A3 = x'yz'$$

$$A4 = x'yz$$


$$A5 = xy'z'$$

$$A6 = xy'z$$


$$A7 = xyz'$$

$$A8 = xyz$$

c.

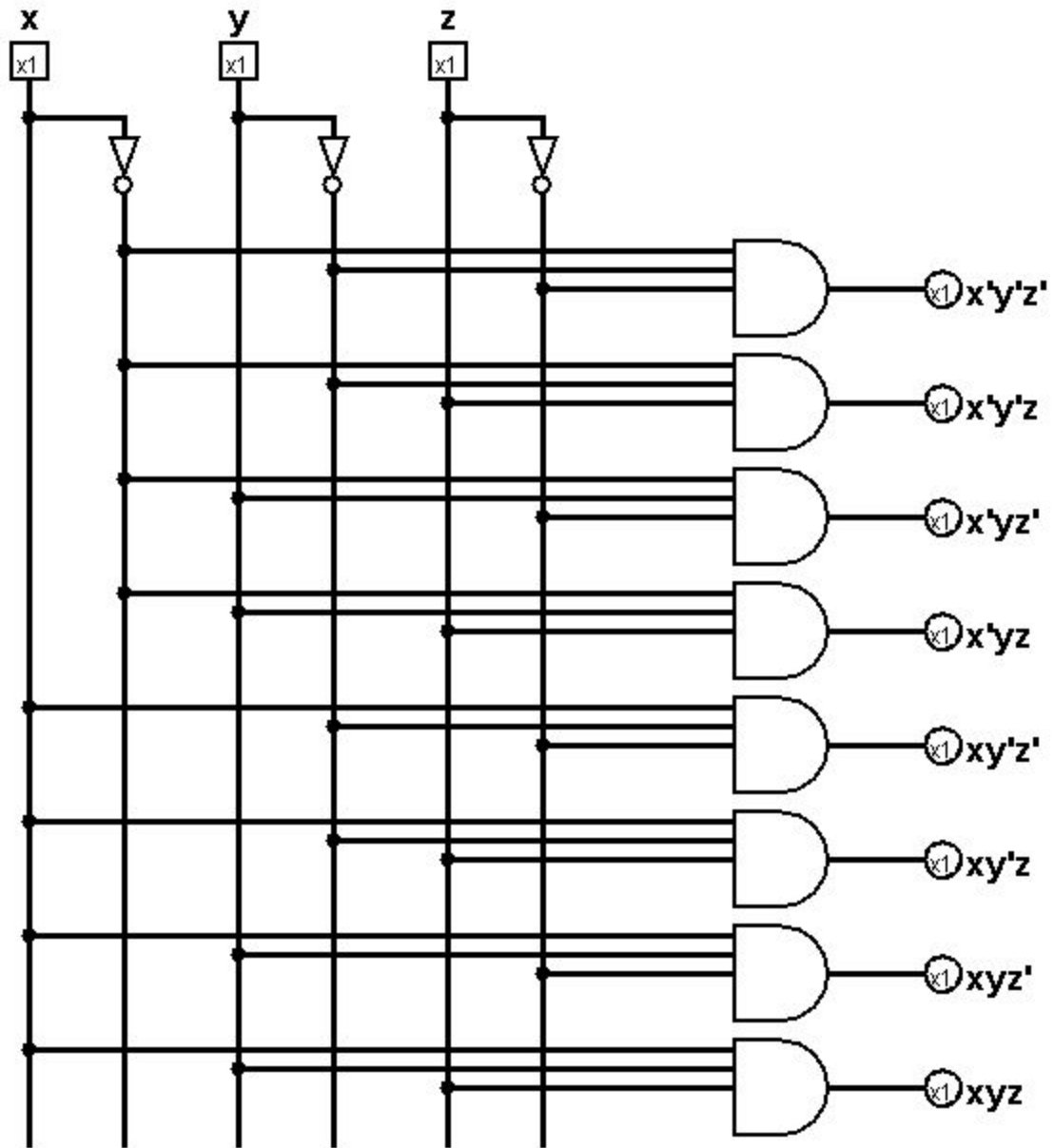

d.

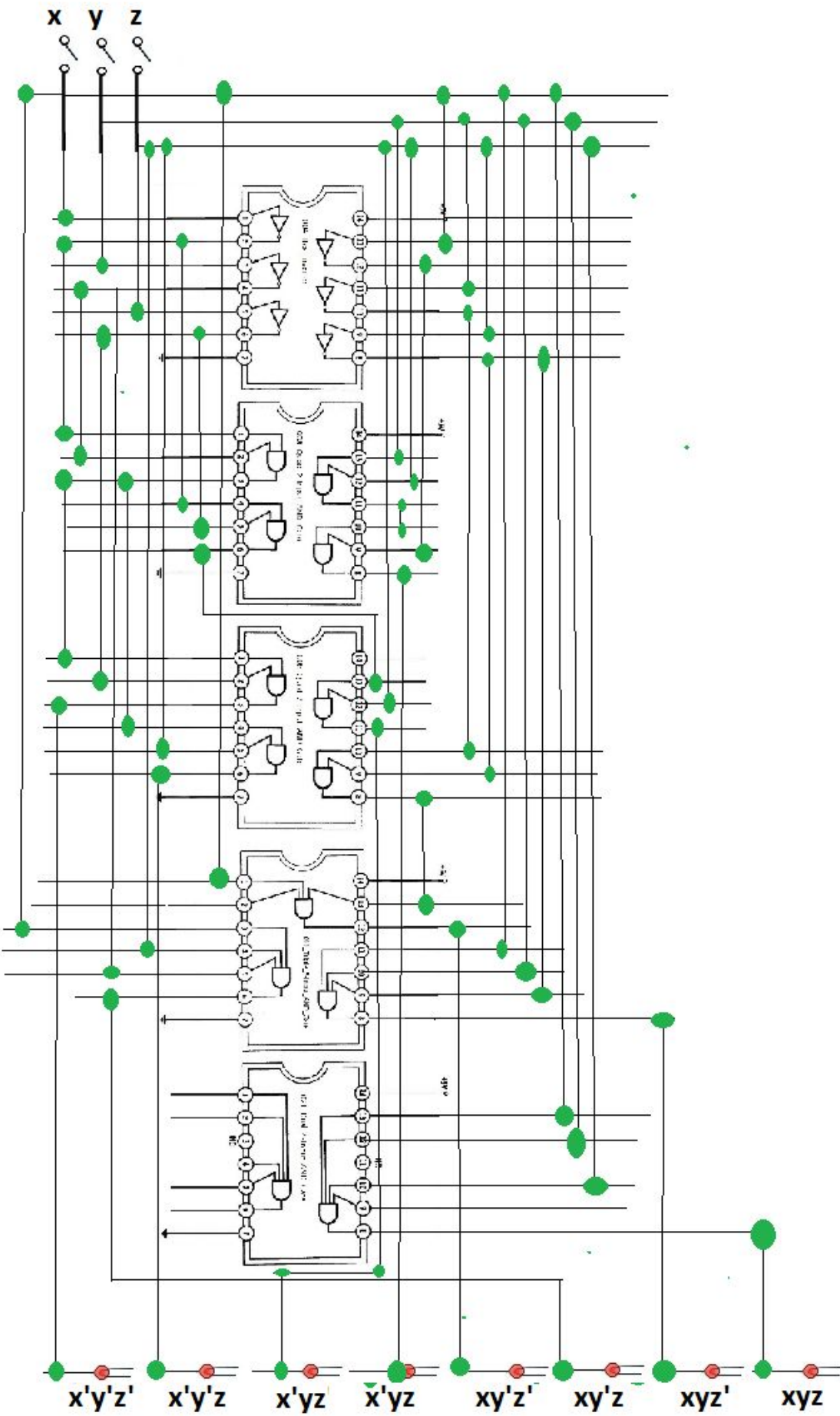

e. Choose: $x'y'z'$, $x'yz'$, xyz .

$x'y'z'$ LED is on when: all the switches are off

$x'yz'$ LED is on when: x,y switches are off and y switch is on

xyz LED is on when: x,y, and z switches are on

I choose the value randomly

4. The difference is that the result of the decoder chip is inversed compared to 2-to-4 decoder.

For example, with 2-to-4 decode, when x and y = 1, only 1 LED is on. However, with the decoder chip, with x and y = 1, 3 LEDs are on, and the off one is xy.

5.

